



Electronics Science

Miss. Karle.P.S



Combinational Logic

- Combinational Logic:
 - Output depends only on current input
 - Has no memory


Sequential Logic

- Sequential Logic:
 - Output depends not only on current input but also on past input values, e.g., design a counter
 - Need some type of memory to remember the past input values

Sequential Circuits

Circuits that we
have learned
so far

Information Storing
Circuits

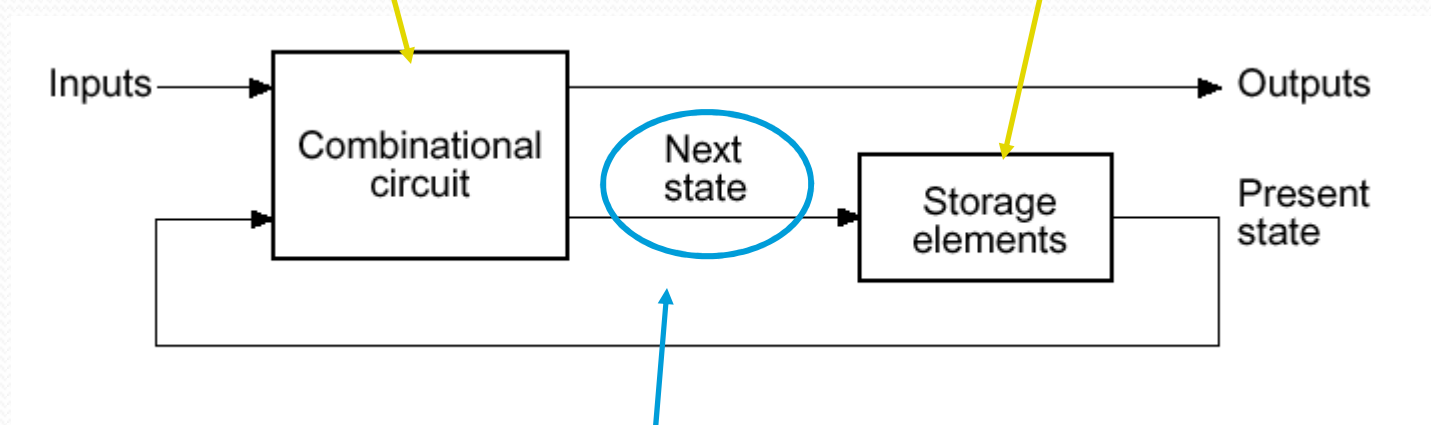

Timed "States"

Sequential Logic: Concept

- Sequential Logic circuits remember past inputs and past circuit state.
- Outputs from the system are “fed back” as new inputs
 - With gate delay and wire delay
- The storage elements are circuits that are capable of storing binary information: memory.




Synchronous vs. Asynchronous


There are two types of sequential circuits:

- **Synchronous** sequential circuit: circuit output changes only at some discrete instants of time. This type of circuits achieves synchronization by using a timing signal called the *clock*.
- **Asynchronous** sequential circuit: circuit output can change at **any** time (clock less).

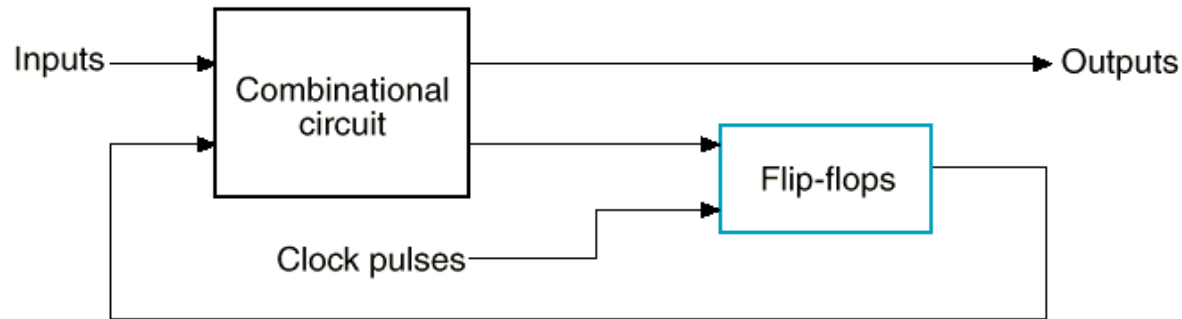Synchronous Sequential Circuits: Flip flops as state memory




(a) Block diagram

 

(b) Timing diagram of clock pulses


- The flip-flops receive their inputs from the combinational circuit and also from a clock signal with pulses that occur at fixed intervals of time, as shown in the timing diagram.

Clock Period

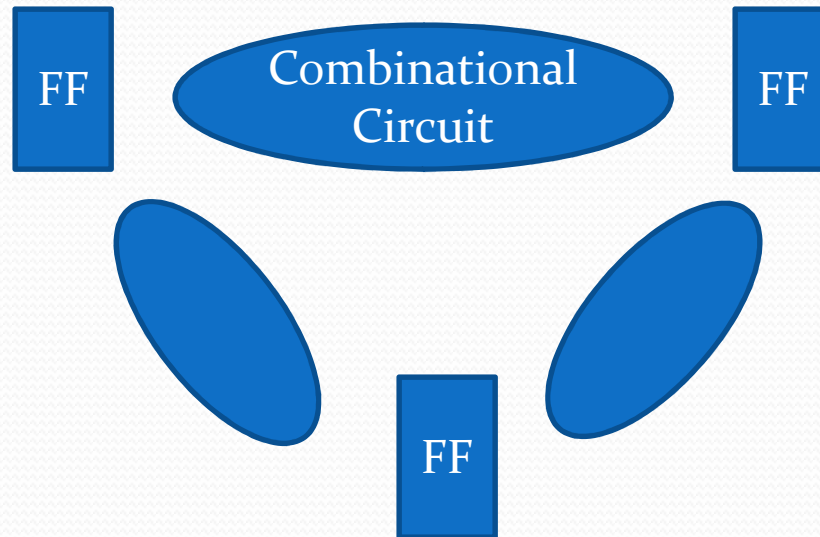

Smallest clock period = largest combinational circuit delay between any two directly connected FF, subjected to impact of FF setup time.

SR Latch (NAND version)

 


S'	R'	Q	Q'
0	0		
0	1	1	0
1	0		
1	1		

Set

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


SR Latch (NAND version)

 

S'	R'	Q	Q'	
0	0			
0	1	1	0	Set
1	0			
1	1	1	0	Hold

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


SR Latch (NAND version)

 

S'	R'	Q	Q'	
0	0			
0	1	1	0	Set
1	0	0	1	Reset
1	1	1	0	Hold

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


SR Latch (NAND version)

 

S'	R'	Q	Q'	
0	0			
0	1	1	0	Set
1	0	0	1	Reset
1	1	1	0	Hold
0	1	0	1	Hold

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


SR Latch (NAND version)

 

S'	R'	Q	Q'	
0	0	1	1	Disallowed
0	1	1	0	Set
1	0	0	1	Reset
1	1	1	0	Hold
0	1	0	1	Hold

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

SR Latch with Clock signal

 

(a) Logic diagram


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

(b) Function table

Latch is sensitive to input changes **ONLY** when $C=1$


D Latch

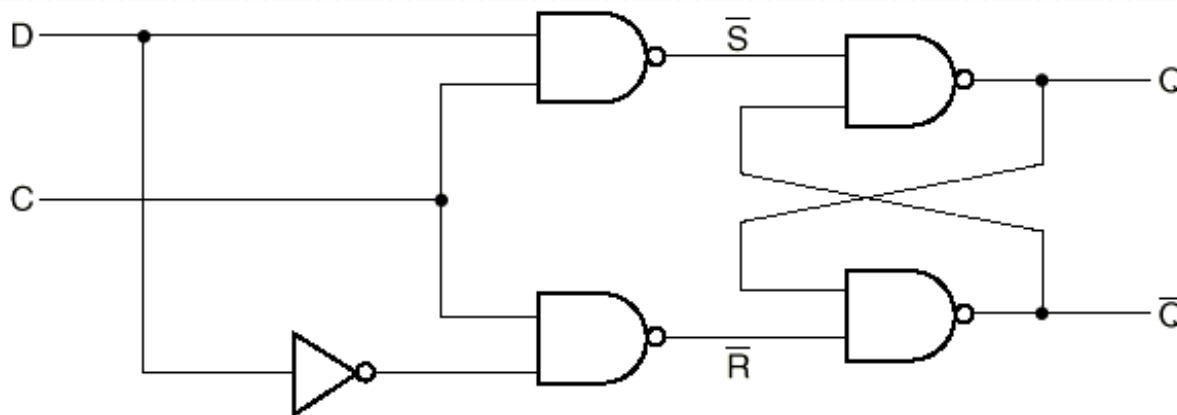- One way to eliminate the undesirable indeterminate state in the RS flip flop is to ensure that inputs S and R are never 1 simultaneously. This is done in the *D latch*:



C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

D Latch with Transmission Gates

 


- $C=1 \rightarrow$ TG1 closes and TG2 opens $\rightarrow Q'=D'$ and $Q=D$
- $C=0 \rightarrow$ TG1 opens and TG2 closes \rightarrow Hold Q and Q'

Flip-Flops

- Latches are “transparent” (= any change on the inputs is seen at the outputs immediately when $C=1$).
- This causes synchronization problems.
- Solution: use latches to create flip-flops that can respond (update) only on specific times (instead of any time).
- Types: RS flip-flop and D flip-flop

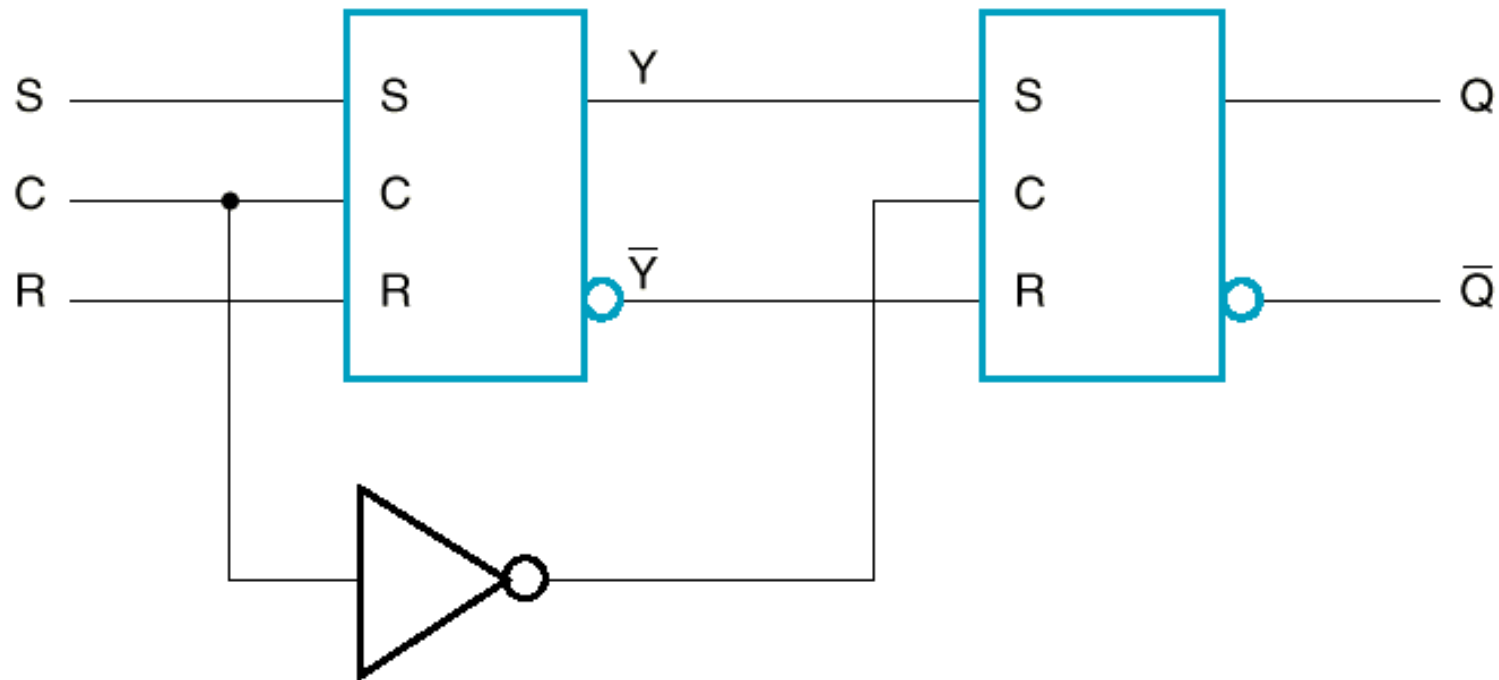
Master-Slave FF configuration using SR latches




Master-Slave FF configuration using SR latches (cont.)

S	R	CLK	Q	Q'	
0	0	1	Q_0	Q_0'	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q_0	Q_0'	Store

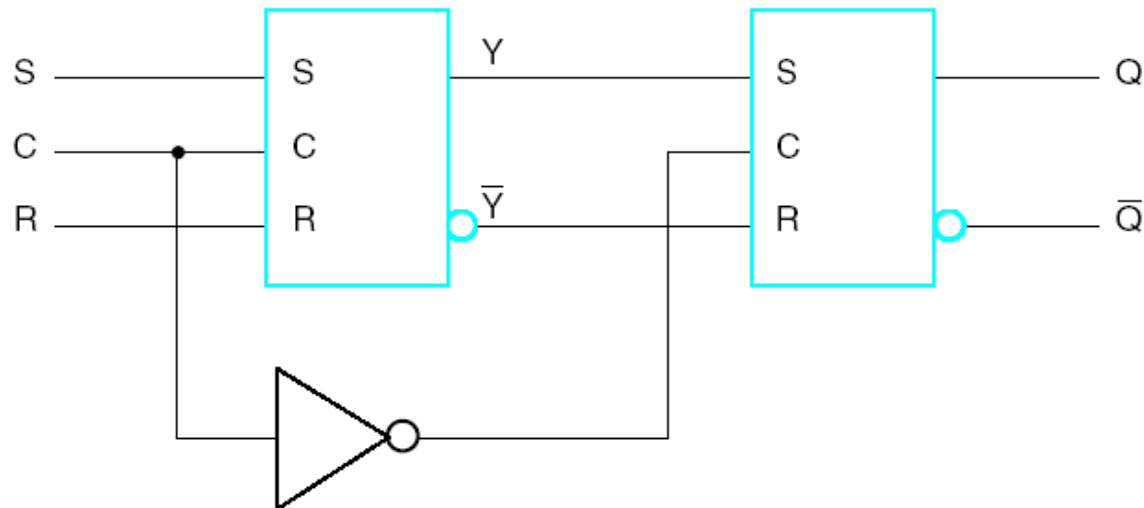- When $C=1$, master is enabled and stores *new* data, slave stores *old* data.
- When $C=0$, master's state passes to enabled slave, master not sensitive to new data (disabled).



D Flip-Flop

 

Characteristic Tables

- Defines the logical properties of a flip-flop (such as a truth table does for a logic gate).
- $Q(t)$ – present state at time t
- $Q(t+1)$ – next state at time $t+1$

Characteristic Tables (cont.)

SR Flip-Flop



S	R	Q(t+1)	Operation
0	0	Q(t)	No change/Hold
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined/Invalid

Characteristic Tables (cont.)

D Flip-Flop		
D	Q(t+1)	Operation
0	0	Set
1	1	Reset

Characteristic Equation: $Q(t+1) = D(t)$

D Flip-Flop

  

Setup time




Sequential Circuit Analysis

- ***Analysis***: Consists of obtaining a suitable description that demonstrates the time sequence of inputs, outputs, and states.
- Logic diagram: Boolean gates, flip-flops (of any kind), and appropriate interconnections.
- The logic diagram is derived from any of the following:
 - Boolean Equations (FF-Inputs, Outputs)
 - State Table
 - State Diagram

 
Example

- Input: $x(t)$
- Output: $y(t)$
- State: $(A(t), B(t))$
- What is the Output
- What is the Next State Function?



 Example (continued)

- Boolean equations functions:
 - $A(t+1) = A(t)x(t)$
 $B(t)x(t)$
 - $B(t+1) = A'(t)x(t)$
 - $y(t) = x'(t)(B(t) + A(t))$



State Table Characteristics

• *State table* – a multiple variable table with the following four sections:

- *Present State* – the values of the state variables for each allowed state.
- *Input* – the input combinations allowed.
- *Next-state* – the value of the state at time (t+1) based on the present state and the input.
- *Output* – the value of the output as a function of the present state and (sometimes) the input.
- From the viewpoint of a truth table:
 - the inputs are Input, Present State
 - and the outputs are Output, Next State

Example: State Table

- The state table can be filled in using the next state and output equations:
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = \bar{A}(t)x(t)$;
 - $y(t) = \bar{x}(t)(B(t) + A(t))$


Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Diagrams

- The sequential circuit function can be represented in graphical form as a state diagram with the following components:
 - A circle with the state name in it for each state
 - A directed arc from the Present State to the Next State for each state transition
 - A label on each directed arc with the Input values which causes the state transition, and
 - A label:
 - On each circle with the output value produced, or
 - On each directed arc with the output value produced.

 Example: State

- Diagram gets confusing for large circuits
- For small circuits usually easier to understand than the state table



Summary

- Sequential circuit timing analysis
- Flip-Flop
 - Transmission gate based flip-flop design
 - Setup time